

1.


Q:- 1

$$\begin{aligned}V_{TM} &= V_{TH0} + \gamma \left( \sqrt{|V_{SB}| + 2\phi_F} - \sqrt{2\phi_F} \right) \\&= 0.6 + 0.4 \left( \sqrt{0.5 + 0.8} - \sqrt{0.8} \right) \\&= 0.6 + 0.4 (1.14 - 0.894) \\&= \underline{\underline{0.698}}\end{aligned}$$

$$\begin{aligned}I_D &= \frac{1}{2} \mu_n C_{ox} \frac{W}{L} \left[ (V_{GS} - V_T) \right]^2 \\&= \frac{1}{2} \times 100 \times 10^{-6} \times 50 \times (0.9 - 0.698)^2 \\&= \underline{\underline{101.77 \mu A}}\end{aligned}$$

2.

Q:-2 small signal model of MOSFET

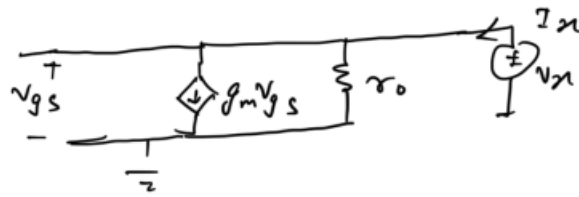

$$R_x = \frac{V_x}{I_x}$$

K.C.L

$$g_m v_{gs} + \frac{V_x}{r_o} = I_x$$

$$V_x - v_{gs} = 0$$

$$v_{gs} = V_x$$

$$g_m V_x + \frac{V_x}{r_o} = I_x$$

$$V_x \left( g_m + \frac{1}{r_o} \right) = I_x$$

$$R_x = \frac{V_x}{I_x} = \frac{1}{\frac{1}{r_o} + g_m}$$

$$= r_o \parallel \frac{1}{g_m} \quad \checkmark$$

3.

Q:-3 For 2.73V to 3.73V at input output should be from 0 to 5V.

For 1V input swing output swing is 5V.

Gain of op-amp = 5.

Let's say <sup>for</sup>  $V_{in} = 3.73V$ .

K.C.L at inverting node:-  $V_{out} = 5V$

$$\frac{3.73 - 5}{R_a} + \frac{3.73}{80k} + \frac{3.73 - 5}{100k} = 0$$

$$\boxed{R_a = 37k}$$

4.

$$I_D = \frac{1}{2} \mu_n C_{ox} \left( \frac{W}{L} \right) (V_{GS} - V_{TH})^\alpha (1 + \lambda V_{DS})$$

$$g_m = \frac{\partial I_D}{\partial V_{GS}}$$

3 marks

$$\Rightarrow g_m = \frac{\alpha}{2} \mu_n C_{ox} \left( \frac{W}{L} \right) (V_{GS} - V_{TH})^{\alpha-1} (1 + \lambda V_{DS})$$

2 marks

$$r_o = \left( \frac{\partial I_D}{\partial V_{DS}} \right)^{-1}$$

3 marks

$$\Rightarrow r_o = \frac{1}{\frac{1}{2} \mu_n C_{ox} \left( \frac{W}{L} \right) (V_{GS} - V_{TH})^\alpha \cdot \lambda}$$


2 marks

5.
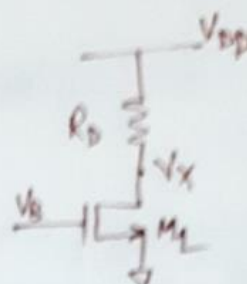
### Q.5. Solution:

For  $M_1$  to be at the edge of the saturation,

$$V_{DS} = V_{GS} - V_{th}$$
$$\Rightarrow V_X = V_B - V_{th} \quad \text{--- (2 marks)}$$



Now,

$$I_D = \frac{V_{DD} - V_X}{R_D} = \frac{1}{2} \mu_n C_{ox} \left( \frac{W}{L} \right) (V_{GS} - V_{th})^2 (1 + \lambda V_{DS})$$
$$\text{--- (2 marks)}$$

$$\Rightarrow \frac{1.8 - V_X}{5 \times 10^3} = \frac{1}{2} \cdot 200 \times 10^{-6} \times \frac{20}{0.18} V_X^2 (1 + 0.1 V_X)$$

$$\Rightarrow V_X^3 + 10 V_X^2 + 0.18 V_X - 0.324 = 0$$

$$\Rightarrow V_X = 0.169 \text{ V} \quad \text{--- (4 marks)}$$

$$\Rightarrow \boxed{V_B = 0.569 \text{ V}} \quad \text{--- (2 marks)}$$

### Note:

- 1) Those who have ignored ' $\lambda$ ' (i.e. taken  $\lambda=0$ ) have been given full marks if they got the answer as  $V_B = 0.571 \text{ V}$
- 2) Those who have taken  $\lambda=0.1$  & left the solution till the cubic equation, have been given full marks if their final cubic equation is correct.

1) Given :-  $R_1 = 100 \text{ k}\Omega$ ,  $C_f = 0.1 \mu\text{F}$ ,  $V_c(\omega) = 0 = V_o(\omega)$

$$\Rightarrow I = \frac{V_i - 0}{R_1} \Rightarrow I = C_f \cdot d\left(\frac{0 - V_o}{dt}\right) = -C_f \frac{dV_o}{dt}$$

$$\Rightarrow \frac{V_i}{R_1} = -C_f \frac{dV_o}{dt} \Rightarrow \frac{dV_o}{dt} = -\frac{V_i}{C_f R_1} \Rightarrow V_o = - \int_0^t \frac{V_i dt}{R_1 C_f} \leftarrow \text{expression of an integrator}$$

$\hookrightarrow (i)$

$$\text{for } 0 \leq t < 1 \rightarrow V_i = 50 \text{ mV}$$
$$1 \leq t < 2 \rightarrow V_i = -50 \text{ mV}$$

By incorporating the change developed on the capacitor:-

$$\Rightarrow V_o(t) - V_o(t_1) = -\frac{1}{R_1 C_f} \int_{t_1}^t V_i dt$$

for  $0 \leq t < 1$  :-  $V_o(0) = 0$

$$\Rightarrow V_o(t) - V_o(0) = -\frac{1}{R_1 C_f} \int_0^t V_i dt = -\frac{1}{100 \times 10^3 \times 0.1 \times 10^{-6}} \int_0^t 50 \times 10^{-3} dt$$

$$\Rightarrow V_o(t) - 0 = -\frac{50 \times 10^{-3}}{10^5 \times 10^{-7}} \times t \Rightarrow \underline{V_o(t) = -5t} \text{ for } 0 \leq t < 1$$

When  $t = 1 \text{ s}$ ,  $V_o(1) = -5 \text{ V} \Leftarrow$  change developed on the capacitor at  $t = 1 \text{ s}$

For  $1 \leq t < 2$  :-  $\Rightarrow V_o(t) - V_o(t_1) = -\frac{1}{R_1 C_f} \int_{t_1}^t V_i dt$

$$\Rightarrow V_o(t) + 5 = -\frac{1}{100 \times 10^3 \times 0.1 \times 10^{-6}} \int_1^t (-50 \times 10^{-3}) dt$$

$$\Rightarrow V_o(t) + 5 = 5 [t]_1^t - 5 \Rightarrow V_o(t) = 5(t - 1) - 5$$


$$\Rightarrow V_o(t) = 5t - 10 \quad \text{for } 1 \leq t < 2$$

$$\text{When } t = 2s \Rightarrow V_o(2) = 0V.$$

$$\text{for } 0 \leq t < 1 \Rightarrow V_o = -(5t)V$$

$$1 \leq t < 2 \Rightarrow V_o = (5t - 10)V$$
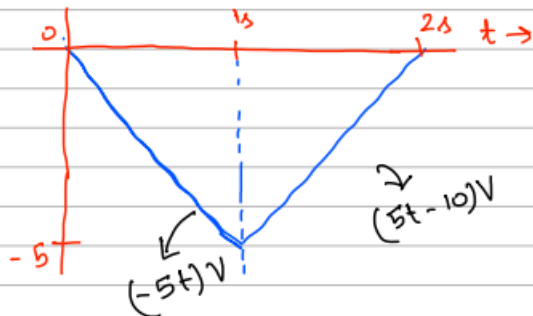
$$\begin{aligned} V_o(0) &= 0V \\ V_o(1) &= -5V \\ V_o(2) &= 0V. \end{aligned}$$



7.

$$2) \Rightarrow I_c = C \cdot \frac{d}{dt} \left( \frac{V_i - 0}{1} \right) = C \frac{dV_i}{dt}$$

$$\Rightarrow I_c = \frac{0 - V_o}{R_f} = -\frac{V_o}{R_f} \Rightarrow C \frac{dV_i}{dt} = -\frac{V_o}{R_f} \Rightarrow V_o = -C R_f \frac{dV_i}{dt}$$

$$\Rightarrow V_o = -2 \times 10^{-6} \times 10 \times 10^3 \times \frac{d}{dt} (30t) = (-2 \times 10^{-2} \times 30)V = -0.6V$$

8.

$$2) \quad V_o = 2V_1 - 3V_2 + 4V_3 - 5V_4$$


The +ve and -ve terms can be added separately using 2 adders and then subtractor can be used.

$$\Rightarrow V_{o1} = -\left(\frac{R_{f1}}{R_1} V_1 + \frac{R_{f1}}{R_3} V_3\right) \Rightarrow \frac{R_{f1}}{R_1} = 2 \Rightarrow \frac{R_{f1}}{R_3} = 4$$

$$\text{Let } R_{f1} = 100\text{k}\Omega, \text{ then } R_1 = 50\text{k}\Omega, R_3 = 25\text{k}\Omega$$

$$\Rightarrow V_{o2} = -\left(\frac{R_{f2}}{R_2} V_2 + \frac{R_{f2}}{R_4} V_4\right) \Rightarrow \frac{R_{f2}}{R_2} = 3 \Rightarrow \frac{R_{f2}}{R_4} = 5$$
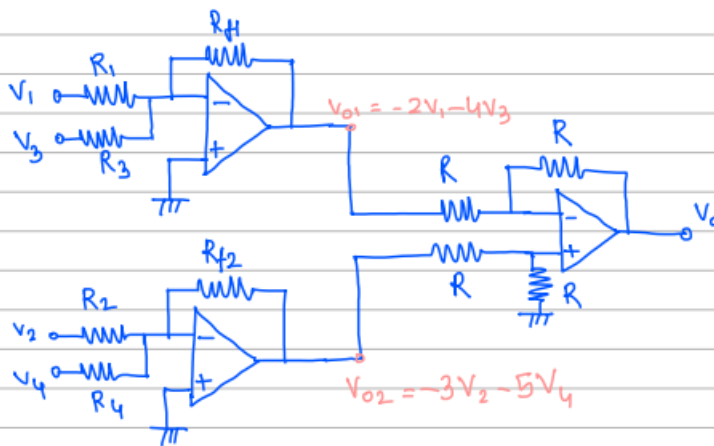
$$\text{Let } R_{f2} = 150\text{k}\Omega \Rightarrow R_2 = 50\text{k}\Omega \Rightarrow R_4 = 30\text{k}\Omega$$



9.

$$3) \text{ For an ideal integrator: } V_o = -\frac{1}{R_i C_f} \int_0^t V_{in} dt$$

$$R_i = 100\text{k}\Omega, C_f = 1\mu\text{F}, V_m = 6\text{mV}, \omega = 2\pi f = 4\pi \times 10^3 \text{ rad/s}$$

$$\Rightarrow V_o = -\frac{1}{100 \times 10^3 \times 1 \times 10^{-6}} \int_0^t 6 \times 10^{-3} \sin(4\pi \times 10^3 t) dt$$

$$\Rightarrow V_o = -0.06 \left[ \frac{-\cos(4\pi \times 10^3 t)}{4\pi \times 10^3} \right]_0^t = 4.77 \times 10^{-6} [\cos(4000\pi t) - 1] \text{ V}$$

(Ans)



10.

a) By symmetry,

$$I_{D1} = I_{D2} = I_{\frac{1}{2}} = 0.2 \text{ mA}, V_{D1} = V_{D2} = 3 - 2.5 \times 0.2 = 2.5 \text{ V}$$

For  $V_{cm} = 2.5$

Assuming the transistors are in saturation, — (2 marks)

$$I_{D1} = \frac{1}{2} \cdot \mu_n C_{ox} \frac{W}{L} (V_{cm} - V_s - V_{th})^2$$

$$200 \times 10^{-6} = \frac{1}{2} \cdot 200 \times 10^{-6} \times 10 \left( \underset{\downarrow}{V_{gs}} - 0.4 \right)^2$$

$$\Rightarrow V_{gs} = 847 \text{ mV} \quad \text{— (2 marks)}$$

b)  $V_s = V_{cm} - V_{gs} = 1.653 \text{ V}$  — (2 marks)

c) For saturation  $V_{D1} > V_{cm} - V_{th}$

$$\therefore \boxed{V_{cm} < 2.9 \text{ V}} \quad \text{— (2 marks)}$$

d) For conduction,  $V_{gs} > V_{th}$

$$\therefore V_{cm} - V_s > V_{th}$$

$$\therefore \boxed{V_{cm} \geq 0.7 \text{ V}} \quad \text{— (2 marks)}$$

Note: Some students have used  $V_{gs} = 847 \text{ mV}$  in part 'd'.  
They have been given full marks.

11.

Q:- (1)

$$g_{m1} = \sqrt{2 I_{D1} \mu_n C_{ox} \left(\frac{W}{L}\right)_1}$$


$$= \sqrt{2 \times 150 \times 10^{-6} \times 60 \times 10^{-6} \times 5}$$

$$= 300 \mu A/V$$

$$g_{m2} = \sqrt{2 I_{D2} \mu_n C_{ox} \left(\frac{W}{L}\right)_2}$$

$$= \sqrt{2 \times 150 \times 10^{-6} \times 60 \times 10^{-6} \times 20}$$

$$= 600 \mu A/V$$

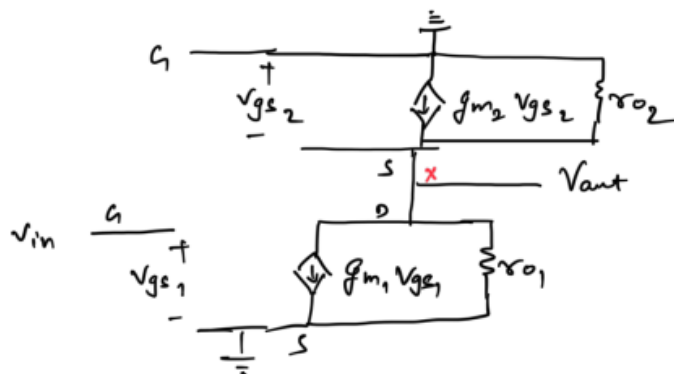

K.C.L at node x

$$g_{m1} V_{gs1} + \frac{V_{out}}{r_{o1}} + \frac{V_{out}}{r_{o2}} - g_{m2} V_{gs2} = 0 \quad \text{--- (ii)}$$

$$V_{in} - V_{gs1} = 0$$

$$V_{in} = V_{gs1} \quad \text{--- (i)}$$

$$-V_{gs2} - V_{out} = 0$$

$$V_{out} = -V_{gs2} \quad \text{--- (ii)}$$

Putting eq. (i) & eq. (ii) in eq. (ii)

$$g_{m1} V_{in} + \frac{V_{out}}{r_{o1}} + \frac{V_{out}}{r_{o2}} + g_{m2} V_{out} = 0$$

$$V_{out} \left( \frac{1}{r_{o1}} + \frac{1}{r_{o2}} + g_{m2} \right) = -g_{m1} V_{in}$$

$$\frac{V_{out}}{V_{in}} = \frac{-g_{m1}}{\frac{1}{r_{o1}} + \frac{1}{r_{o2}} + g_{m2}}$$


$$= \frac{-300 \times 10^{-6}}{600.33 \times 10^{-6}}$$

$$\boxed{\frac{V_{out}}{V_{in}} = -0.499}$$

$$\frac{\frac{1}{6} + \frac{1}{6}}{\frac{2}{6} + 600 \times 10^{-6}}$$

$$\left( \frac{1}{3} + 600 \right)$$

Alternative soln:-

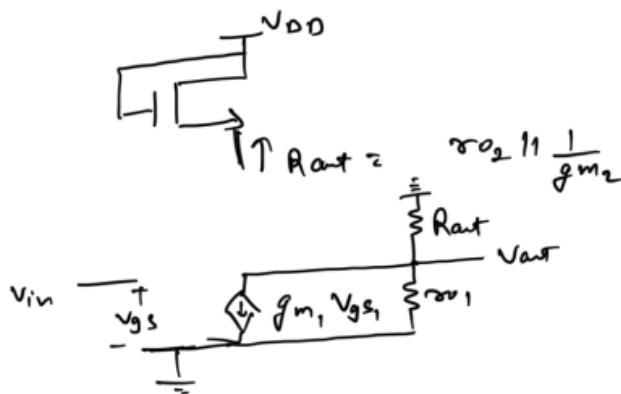

$$\frac{V_{out}}{V_{in}} = -g_{m1} (r_{o1} || R_{ant})$$

$$= -g_{m1} \left( r_{o1} || r_{o2} || \frac{1}{g_{m2}} \right)$$

$$\text{As } (r_{o1} || r_{o2}) \gg \frac{1}{g_{m2}}$$

$$\frac{V_o}{V_{in}} = \frac{-g_{m1}}{g_{m2}} = -0.5 \quad r_{o1} || r_{o2} || \frac{1}{g_{m2}} \approx \frac{1}{g_{m2}}$$

12.

Sol<sup>n</sup>

$V_0 = E_{CA}(30^\circ\text{C}) + E_{BA}(T) + E_{BC}(0^\circ\text{C})$  — (1)  
 $E_{CA}(30^\circ\text{C}) = E_{CB}(30^\circ\text{C}) - E_{AB}(30^\circ\text{C}) = 1.196 - 1.801 = -0.605 \text{ mV}$   
 $E_{BC} = 0 \text{ V}, \quad V_0 = 26.74 \text{ mV}$


Shot on OnePlus  
 2023.11.17 23:52

from eq (1)  
 $26.74 = -0.605 + E_{BA}(T) + 0$   
 $E_{BA}(T) = 27.345 \text{ mV}$   
 from table,  $T = 380^\circ\text{C}$

Shot on OnePlus  
 2023.11.17 23:52

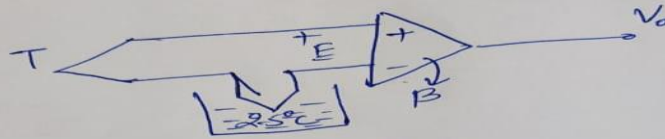13.

→ Soln → 11a) Given,  $\beta = 1000$   
 $V_o = 2.050$   
 $T = ?$



$$E = S(T_H - T_c)$$

$$E = S(T - 25^\circ\text{C}) \quad \text{--- ①}$$

$$E = V_{in} \quad \text{--- ②}$$

$$V_o = V_{in} \times \beta$$

$$2.050 = V_{in} \times 1000$$

$$V_{in} = 2.050 \times 10^{-3} \text{ V}$$

from eq-① & ②

$$2.050 \times 10^{-3} = 41 \times 10^{-6} (T - 298)$$

$$T - 298 = \frac{2.050 \times 10^{-3}}{41 \times 10^{-6}}$$

$$T - 298 = \frac{2.050 \times 10^{-3}}{41 \times 10^{-6}}$$

$$T - 298 = \frac{2.050 \times 10^{-3}}{41 \times 10^{-6}} \Rightarrow T = 50 + 298$$

$$T = 348 \text{ K} \Rightarrow \boxed{T = 75^\circ\text{C}}$$

14.

→ Soln → ①a)  $\beta = 25$ ,  $V_o = 96 \text{ mV}$

$$\theta_{ref} = 0$$

$$S = 40 \mu\text{V}/^\circ\text{C}$$

$$\theta = ?$$

$$E = S(\theta - \theta_{ref}) \quad \text{--- ①}$$

$$E = V_{in}$$

$$V_o = \beta \times V_{in}$$

$$V_{in} = \frac{96}{25} = 3.84 \text{ mV}$$

$$\theta = \frac{3.84 \text{ mV}}{40 \mu\text{V}} + 0$$

$$\boxed{\theta = 96^\circ\text{C}}$$

Ans